

"010" – Move instruction
 "000" – Add instruction
 "001" – Subtraction
 "011" – Jump if zero instruction
 "100" – Multiply instruction

```

"0100100000011",-- Mov R2, 3
"0101110000010",-- Mov R7, 2
"0011110100000",-- Sub R7,R2
"1011110000000",-- Neg R7
"0100110000010",-- Mov R3, 2
"0001110110000",-- Add R7, R3
"1001110110000",-- Mul R7, R3
"0110000000001"-- JmZ( check R0 )
  
```

```

"0101110000001", --Mov R7, 1
"0100100000010", --Mov R2, 2
"0001110100000", --Add R7, R2
"0100110000011", --Mov R3, 3
"0001110110000", --Add R7, R3
"0111110000001", --JmZ R7, 1
"0001110000000", --Add R7, R0
"0110000000110" --JmZ R0, 6
  
```

```

library IEEE;
use IEEE.STD_LOGIC_1164.ALL;

entity Instruction_Decoder is
    Port ( I : in STD_LOGIC_VECTOR (12 downto 0);
          Reg_Check_Jump : in STD_LOGIC_VECTOR (3 downto 0);
          Load_Select : out STD_LOGIC;
          Imm_Value : out STD_LOGIC_VECTOR (3 downto 0);
          Reg_Enable : out STD_LOGIC_VECTOR (2 downto 0);
          Reg_Select_1 : out STD_LOGIC_VECTOR (2 downto 0);
          Reg_Select_2 : out STD_LOGIC_VECTOR (2 downto 0);
          Add_Sub : out STD_LOGIC;
          Jump_Flag : out STD_LOGIC;
          Address : out STD_LOGIC_VECTOR (2 downto 0);
          Mul: out STD_LOGIC
    );
end Instruction_Decoder;

```

architecture Behavioral of Instruction_Decoder is

component Mux_2_to_1_3bit

```

    Port ( Sel : in STD_LOGIC;
          D0 : in STD_LOGIC_VECTOR (2 downto 0);
          D1 : in STD_LOGIC_VECTOR (2 downto 0);
          Y : out STD_LOGIC_VECTOR (2 downto 0));
end component;

```

```

signal Ins : STD_LOGIC_VECTOR (2 downto 0);
signal RegA : STD_LOGIC_VECTOR (2 downto 0);
signal RegB : STD_LOGIC_VECTOR (2 downto 0);
signal Data : STD_LOGIC_VECTOR (3 downto 0);
signal Sel: STD_LOGIC;

```

begin

```

Ins <= I(12 downto 10);
RegA <= I(9 downto 7);
RegB <= I(6 downto 4);

```

```

with Ins select Reg_select_1<=
    "000" when "101",
    RegA when others;

```

```

with Ins select Reg_select_2<=
    RegA when "101",
    RegB when others;

```

```

Data <= I(3 downto 0);

```

```

Sel <= NOT(Ins(1)) AND Ins(0);

```

```

Load_Select <= Ins(1) AND NOT (Ins(0)) ;

```

```

Add_Sub <= Ins(0);

```

```

Jump_Flag <= Ins(1) AND Ins(0) AND NOT( Reg_Check_Jump(3)
    OR Reg_Check_Jump(2) OR Reg_Check_Jump(1)OR Reg_Check_Jump(0));

```

```

Reg_Enable <= RegA;

```

```

Imm_Value <= Data;

```

```

Address <= Data(2 downto 0);

```

```

Mul <= Ins(2) and not(Ins(0)) and not(Ins(1));

```

end Behavioral;

```

library IEEE;
use IEEE.STD_LOGIC_1164.ALL;

entity Slow_Clk is
    Port ( Clk_in : in STD_LOGIC;
           Clk_out : out STD_LOGIC);
end Slow_Clk;

architecture Behavioral of Slow_Clk is

    signal count : integer := 1;
    signal clk_status : std_logic := '0';



begin
    process (Clk_in) begin
        if (rising_edge(Clk_in)) then
            count <= count + 1;
            if (count = 100000000) then
                clk_status <= not clk_status;
                Clk_out <= clk_status;
                count <= 1;
            end if;
        end if;
    end process;
end Behavioral;

```

```

Register_4bit_0 : Register_4bit
PORT MAP(
    D => "0000",
    En => Y(0),
    Clk => Clk,
    Reset => Reg_S,
    Q => R0
);

```

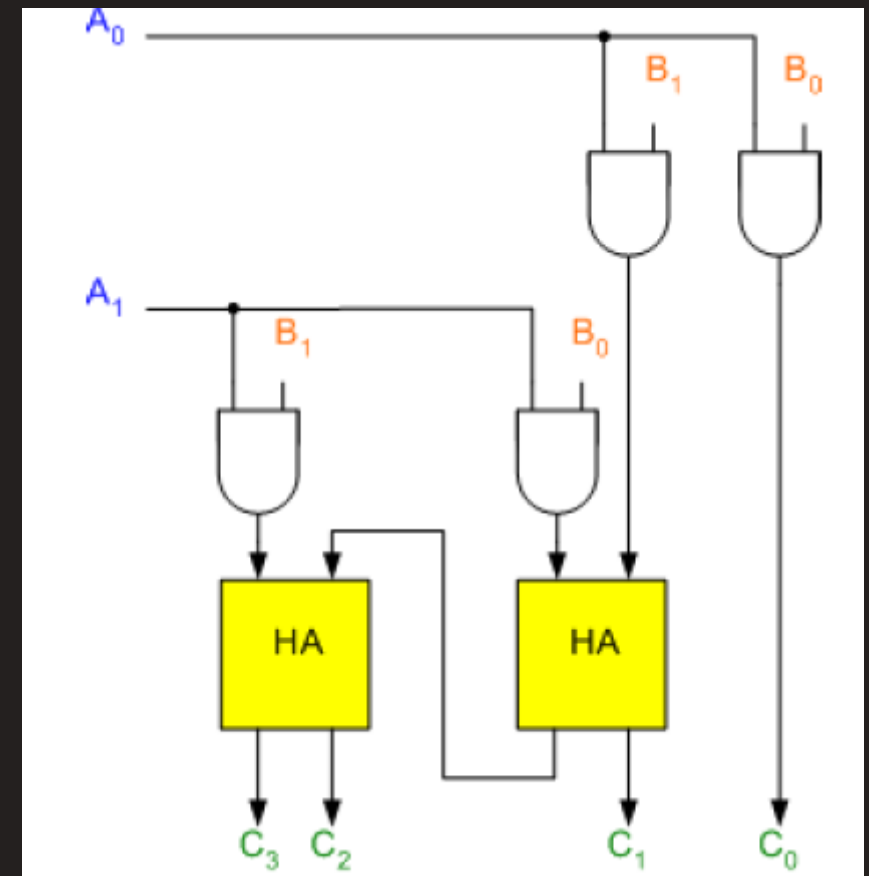 

LUT Count

Site Type	Used	Fixed	Available	Util%
Slice LUTs*	39	0	20800	0.19
LUT as Logic	39	0	20800	0.19
LUT as Memory	0	0	9600	0.00
Slice Registers	49	0	41600	0.12
Register as Flip Flop	49	0	41600	0.12
Register as Latch	0	0	41600	0.00
F7 Muxes	0	0	16300	0.00
F8 Muxes	0	0	8150	0.00